
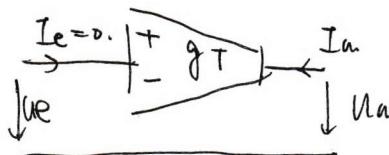


## J. Transkonduktionsverstärker

### J.1 Moden.

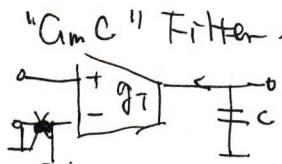

### J.2 应用.



$$\text{OTA} \Rightarrow \tau = \frac{C}{g_T}$$

$$\text{OPV: } \tau = R_C.$$


$$I_a = g_T U_e.$$

- 非线性失真.


-  $T_a$ ,  $I_a$  有界

- 速度高并有 hFQ

"GmC" Filter.

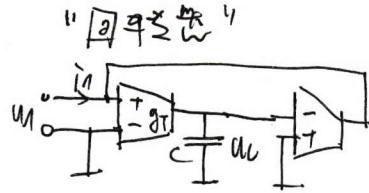

"GmC"

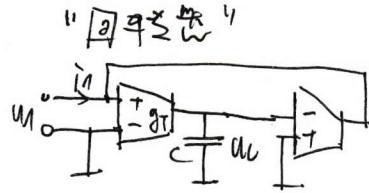

$$U_c = \frac{1}{j\omega C} I_1, \quad i = \frac{dI}{dt} = \frac{CdU}{dt} \Rightarrow I_1 = C \cdot \omega U_c$$

$$U_c = \frac{-g_T U_a}{sC}, \quad I_1 = -g_T U_a$$

$$\Rightarrow Z_1 = \frac{U_a}{I_1} = \frac{sC \cdot g_T}{1 + g_T sC} = S \cdot \frac{C}{g_T^2}$$

由容元件变成纯感.

### J.3 Transistor als Elementar

$$\text{双极管} \quad I_a = I_s \exp\left(\frac{U_e}{U_T}\right) \quad g_T = \frac{I_a A}{U_T}$$

NMOS. 可变阳极电容.

$$I_D = \frac{\beta}{2} (U_{DS} - U_{TH})^2 (1 + \alpha U_{DS}), \text{ 互导效应可忽略}$$

$$g_T = \sqrt{2\beta \cdot I_D A (1 + \alpha U_{DS})}, \approx \sqrt{2\beta I_D A} = g_m$$

恒定电容.

$$I_a = I_D = \beta \left[ (U_e - U_{TH}) U_{DS} - \frac{U_{DS}^2}{2} \right]$$

$$g_T = j_n = \beta \cdot U_{DS}$$

问题(1) 增大增益. 1. 非线性 2. T, Tg. 3. 零点漂移

### J.4 Schaltungseigenschaften

#### J.4.1 差分放大器

$$I_a = I_1 - I_2 = I_0 \tanh \frac{U_e - I_a \frac{P_E}{2}}{2U_T}, \text{ 当无PE时. } g_T = \frac{\partial I_0}{\partial U_e} |_{U_e=0} = \frac{I_0}{2U_T} = \frac{I_0}{U_T}$$

$$\text{求差导. } F(I_a, U_a) = I_0 \tanh \frac{U_e - I_a \frac{P_E}{2}}{2U_T} - I_a = 0.$$

令  $U_e = U_1 + x, \quad U_a = U_2 + x$

$$I_0 \cdot \frac{1}{2U_T} \cdot \left( U_e - I_a \frac{P_E}{2} \right) - I_a = 0$$

$$\frac{I_0}{2U_T} dU_e - \left( \frac{I_0 P_E}{4U_T} + I_a \right) dU_a = 0 \Rightarrow \frac{dI_a}{dU_e} = \frac{I_0}{2U_T} \cdot \frac{4U_T}{I_0 P_E + 4U_T} = \frac{2I_0}{I_0 P_E + 4U_T} = \frac{g_T}{1 + g_T \frac{P_E}{2}}$$

$$\text{由 } \frac{A}{1+AF} \approx 1. \quad AF = g_T \cdot \frac{P_E}{2}, \quad \text{即 } g_T \text{ 不随 } P_E \text{ 变.}$$

$$I_a = \alpha_0 U_e + \alpha_2 U_e^2 + \alpha_3 U_e^3, \Rightarrow \begin{cases} \alpha_1 = g_T / (1 + g_T \frac{P_E}{2}) \\ \alpha_2 = 0 \end{cases}$$

$$\alpha_3 = -\frac{g_T'}{12U_T^2} (1 - \frac{P_E}{2} g_T')^3, \quad g_T' \text{ 不随 } \alpha_1.$$

$$\textcircled{1} HP_3 = \frac{1}{4} \left| \frac{\partial \alpha_3}{\partial U_e} \right| U_e^2 \approx \frac{1}{48} \left( 1 + R_E \cdot \frac{g_T}{2} \right)^3 \left( \frac{U_e}{U_T} \right)^2, \quad \text{闭环(有反馈)}$$

$$\textcircled{2} HP_3 = \frac{1}{48} \left( \frac{U_e}{U_T} \right)^2, \quad \text{开环(无反馈)}$$

$$\text{由 } \textcircled{1} \text{ 得. } \quad \beta_E = \frac{g_T^2}{g_T'} \left[ \frac{1}{12} \left( \frac{48 (HP_3)^2}{U_e^2} \right) \left( \frac{U_e}{U_T} \right)^2 \right] \quad \left( \frac{1}{1 + R_E \cdot \frac{g_T}{2}} \right) = (1 - R_E \cdot g_T')$$

从中间解得  $I_o$ , 我们需要先推导出  $P_E \cdot g_T'$ , 这样

$$P_E \cdot g_T' = 2 \left[ 1 - \frac{3}{4} \frac{48 \cdot H D_3 \cdot (\frac{U_e}{U_T})^2}{I_o} \right], \text{ 成绩说 } I_o \text{ 和 } H D_3 \text{ 是成反比的}$$

$$\text{由 } 1 + g_T \cdot \frac{P_E}{2} = \frac{g_T'}{g_T} \Rightarrow \cancel{g_T' + g_T \cdot \frac{1}{2} \cancel{P_E \cdot g_T}} = \cancel{g_T}. \quad 1 + \frac{P_E}{2} \cdot g_T = \frac{I_o}{2 U_T g_T}$$

$$\Rightarrow I_o = 2 U_T \cdot g_T' (48 H D_3)^{\frac{1}{3}} \left( \frac{U_e}{U_T} \right)^{\frac{2}{3}}$$

#### J. 4.2. CMOS 差分放大器

$$\text{先打号子下. } I_a = I_{a+} - I_{a-}$$

$$U_e = U_{gs1} - U_{gs2}, \quad I_a = \beta \frac{1}{2} (U_{gs} - U_{th})^2 \Rightarrow U_{gs} = \sqrt{\frac{2\beta}{I_{ao}}} + U_{th}$$

$$= \sqrt{\frac{2\beta}{I_{a1}}} - \sqrt{\frac{2\beta}{I_{a2}}} = \frac{\frac{2\beta}{I_{a1}} - \frac{2\beta}{I_{a2}}}{\sqrt{\frac{2\beta}{I_{a1}}} + \sqrt{\frac{2\beta}{I_{a2}}}} = \frac{\frac{2\beta (I_{a2} - I_{a1})}{I_{a1} \cdot I_{a2}}}{\sqrt{2\beta} \left( \frac{1}{\sqrt{I_{a1}}} + \frac{1}{\sqrt{I_{a2}}} \right)} = \frac{\sqrt{2\beta} (I_{a2} - I_{a1})}{\sqrt{2\beta} \cdot (\sqrt{I_{a1} \cdot I_{a2}} + I_{a1} + I_{a2})}$$

$$I_{a1} + I_{a2} = I_o.$$

$$\Rightarrow I_{ao} = I_{a1} + I_{a2} =$$

$$I_{a2} - I_{a1} = \frac{1}{\sqrt{2\beta}} \cdot U_e \cdot \sqrt{I_{a1} I_{a2}} (I_{a1} + I_{a2})$$

$$= I_{a2} - I_{a1} = \frac{I_o}{\sqrt{2\beta}} \cdot U_e \cdot \frac{1}{2} \cdot \frac{\beta}{2} \cdot [U_{gs1} - U_{th}] [U_{gs2} - U_{th}]$$

$$\Rightarrow \sqrt{\beta} I_o \cdot U_e \cdot \sqrt{1 - \frac{\beta}{4 I_o} U_e^2}, \quad U_{gs} = 0. \quad I_{aA} = 0.$$


$$I_a = \alpha_1 U_e + \alpha_2 U_e^2 + \alpha_3 U_e^3$$

$$\rightarrow \alpha_1 = g_T = \sqrt{\beta I_o} \quad H D_3 = \frac{1}{4} \left| \frac{\alpha_2}{\alpha_1} \right| U_e^2 = \frac{1}{32} \frac{\beta}{I_o} U_e^2, \quad g_T = \sqrt{\beta I_o}$$

$$\alpha_2 = 0 \quad I_o = g_T \cdot U_e \sqrt{\frac{1}{32 H D_3}}, \quad \beta = \frac{g_T}{U_e} \sqrt{32 H D_3}$$

$$\alpha_3 = -\frac{1}{3} \frac{\beta^3}{I_o}$$
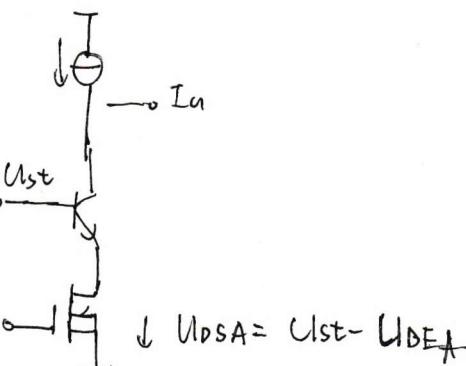
#### J. 4.3. BiCMOS - Transistorstrukturverstehen





$$I_D = \beta \left[ (U_{ds} - U_{th}) U_{ds} - \frac{U_{ds}^2}{2} \right]$$

$$g_n = \beta U_{DSAT}$$

$$\downarrow U_{DSAT} = U_{st} - U_{DEA}$$

#### J. 4.4.

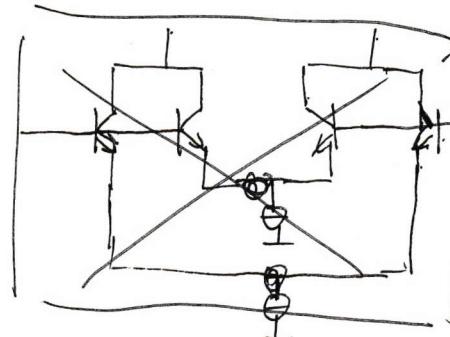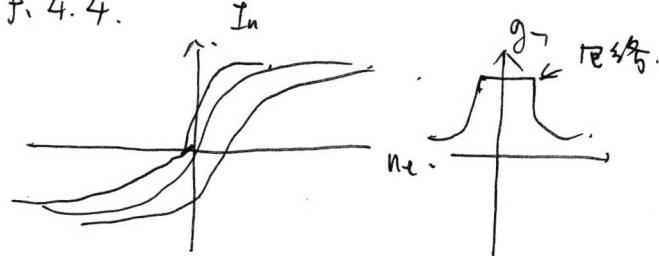

见笔记.

不同的管子模型.

~~从单管放大器到双极性输出的增益~~ (2)

$$1 + g_T \cdot \frac{R_E}{2} = \text{或 } g_T / g_T' = \frac{1}{2U_T \cdot g_T'}$$

$I_o =$

TK-01.

$$1) g_T = \frac{I_{CA}}{U_T} = \frac{I_o}{2U_T} = 1. P_2 \text{ ms}$$

$$I_{CA} = g_T U_e \Rightarrow U_e = U_T = 26 \text{ mV}$$

$$HD_3 = \frac{1}{48} (1)^3 \cdot 1^2 = \frac{1}{48}$$

$$2) HD_3' = \frac{1}{48} \left(1 - \frac{R_E}{2} - g_T'\right)^3 \left(\frac{U_e}{U_T}\right)^3 = \frac{1}{480}$$

$$\frac{R_E}{2} - g_T' = \frac{1}{48}$$

$$1 - \frac{R_E}{2} \cdot g_T' = 1 - \frac{R_E}{2} \cdot \frac{g_T}{1 + g_T \cdot \frac{R_E}{2}} = \frac{1}{1 + g_T \cdot \frac{R_E}{2}}$$

$$\boxed{1 - \frac{R_E}{2} \cdot g_T' = \left(\frac{1}{A_0}\right)^{\frac{1}{3}}}$$

$$R_E \cdot g_T' = \left[1 - \left(\frac{1}{A_0}\right)^{\frac{1}{3}}\right] \frac{2}{g_T}, \quad \left(\frac{1}{1 + g_T \cdot \frac{R_E}{2}}\right)^{\frac{1}{3}} = \left(\frac{1}{A_0}\right)^{\frac{1}{3}} \quad PE \Rightarrow \frac{2 \sqrt[3]{A_0} - 2}{g_T}$$

A0

$$R_E = \frac{1.25}{2.473} \text{ k}\Omega$$

$$g_T' = \frac{g_T}{1 + g_T \cdot \frac{R_E}{2}} = 0. \cancel{+} \text{ ms}$$

8P2.

$$3) g_{T(3)} = 2g_T = 3 \cdot P_4 \text{ ms}$$

$$g_{T(3)} = 1.16 \text{ ms}$$

$$g_T' = \frac{g_T}{1 + g_T \cdot \frac{R_E}{2}} = \frac{1}{g_T \cdot \frac{R_E}{2}}$$

$$g_T \rightarrow \infty \quad g_T' = \frac{2}{R_E} = 1.67 \text{ ms} \Rightarrow HD_3 = \frac{1}{48} \left(1 - \frac{R_E}{2} - g_T'\right)^3 \left(\frac{U_e}{U_T}\right)^3 = 0.0058 < \frac{1}{480}$$

TK-02.

$$1) HD_3 = \frac{1}{32} \cdot \frac{P}{I_o} \cdot U_e^2 \rightarrow \beta = \pm 1.2 \frac{\text{mA}}{\text{V}^2}$$

$$I_n = g_T U_e = \sqrt{\beta I_o}, \quad \beta = \pm 6.6 \text{ mA}$$

$$2) g_T = \sqrt{\beta I_o} \rightarrow \beta = \frac{g_T^2}{2I_o} \rightarrow HD_3 = \frac{1}{32} \cdot \frac{g_T^2}{I_o^2} U_e^2, \quad \text{verringert um Faktor 4}$$

TK-03.

$$1) I_T + I_G + 2nI_D = I_o$$

$$0 \leq I_T + I_G = (1 - 2n)I_D \leq I_o$$

$$0 \leq n \leq 0.5$$

TK-03 请参见 Einstellungschartung 以及相关设置，在 MOS 仿真中，该参数设为  $- \frac{g_{m1}}{g_{m2}} = \sqrt{n_1 n_2 / (n_1 + n_2)}$ ，若扩大增益，则  $|V_{GS}|$  变小，而  $g_{m2} \downarrow$  且  $|V_{GS}|$  变大，从而  $|V_{GS} - V_{THP}|$  会增大。而在两个并联的源极跟随器，减小了第二级 MOS 管的增益。从而在不改变反馈元件的情况下，当  $g_{m1} \cdot g_{m2} = 0.4$  时， $I_{D2} = \frac{1}{3} I_{D1}$ ， $\Rightarrow g_{m2} = \frac{4}{3} g_{m1}$ ， $\checkmark$

$$2) V_i = \frac{I_3 - I_4}{I_1 - I_2} = \frac{I_3 - I_4}{I_T - I_0} = \frac{\sqrt{\beta_A \cdot I_0} \cdot U_{BE} \cdot \sqrt{1 - \frac{\beta_A \cdot U_{BE}^2}{4 \cdot I_0}}}{\sqrt{\beta_B \cdot I_{0A}} \cdot U_{BE} \cdot \sqrt{1 - \frac{\beta_B \cdot U_{BE}^2}{4 \cdot I_{0A}}} \cdot U_{BE}^2}, \quad I_{0A} = I_0 - 2nI_0$$

$$\beta_A \approx I_0, \beta_B \approx I_{0A}. \quad \frac{\beta_A}{\beta_B} = \frac{I_0}{I_{0A}} = \frac{1}{1-2n} \Rightarrow V_i \rightarrow n = \frac{1}{2} (1 - \frac{1}{V_i})$$

$$3) \boxed{V_i = \frac{\sqrt{\beta_A I_0} \cdot U_{BE} \cdot \sqrt{1 - \frac{\beta_A \cdot U_{BE}^2}{4 \cdot I_0}}}{\sqrt{\beta_B I_{0A}} \cdot U_{BE} \cdot \sqrt{1 - \frac{\beta_B \cdot U_{BE}^2}{4 \cdot I_{0A}}} \cdot U_{BE}^2}}$$

Kleinsignal.  $\rightarrow g_T = \sqrt{\beta} \cdot I_0$ .

$$I_{0A} = V_i \cdot g_T \Rightarrow U_{BE} = V_i \cdot \sqrt{\beta_A I_0} \cdot U_{BE}$$

$$\Rightarrow \beta_C = \frac{I_0}{|V_i \cdot U_{BE}|}$$

$$HD_3 = \frac{1}{32} \cdot \frac{1}{(V_i)^2} = \frac{1}{32} \cdot \frac{1}{(1-2n)^2}$$

$$4) \quad n = \frac{1}{2} (1 - \frac{1}{V_i}) = \frac{1}{4}$$

$$HD_3 = \frac{1}{32} \cdot \frac{1}{4} = \frac{1}{128}$$

$$\frac{1}{W_L} k_p = \frac{I_0}{|V_i \cdot U_{BE}|^2} / k_p = 100$$

TK-04.

$$1) \boxed{0 \leq U_{DS} < U_{DS} = U_{DS} < U_{th} \quad (U_{DS} > U_{DS})} \quad U_0 = U_{BEA} + U_{PSA} = 1.1V$$

$$\boxed{0 \leq U_{BE} - (U_0 - U_{BEA}) \leq U_{th}} \quad I_0 = I_D = \beta [U_{BE} - U_{th}] \cdot U_{DS} - U_{DS}/2]$$

$$\boxed{U_0 - U_{BE} + U_{DS} \leq U_{BE} + U_{BEA} - U_{th}} \quad \rightarrow \beta = 606 \cdot \sqrt{\frac{1}{V_T^2}} \rightarrow \frac{1}{V_T} = \beta/k_p = 6.66$$

$$2). \quad g_T = \frac{dI_a}{dU_{BE}} = \beta (U_0 - U_{BEA}) = 182 \text{ mA/V.} \quad g_T \approx I_D$$

$$3) \quad g_T = \frac{dI_a}{dU_{BE}} = \left[ \frac{-F'(U_T)}{F(U_T)} \right]^{-1} = \left( - \frac{I_a \cdot \frac{-P_E}{2V_T} - 1}{I_a \cdot \frac{1}{V_T}} \right)^{-1} = \left( \frac{1 + g_m \cdot P_E}{g_m} \right)^{-1} = \frac{g_m}{1 + g_m P_E}$$

$$4) \quad U_{BE} \geq U_{BE} - U_{th} - U_0 \text{ V}$$

$$U_{BE} \geq U_0 + U_{th} - U_{BE} \text{ V}$$

$$U_{BEA} = 1.1V$$

$$\alpha_2 = \frac{1}{2} \cdot \frac{(1+g_m P_E) g_m^2 \cdot g_m - g_m' m P_E \cdot g_m}{(1+g_m P_E)^2} = \frac{g_m' m}{(1+g_m P_E)^2}$$

$$U_{BE, max} = 0.4V$$

$$g_m = \frac{I_a}{U_T} \Rightarrow g_m' = \frac{1}{U_T} \cdot \frac{g_m}{1+g_m P_E} = \frac{1}{2U_T} \cdot \frac{g_m}{(1+g_m P_E)^2}$$

$$I_{a, max} = 72.7mA$$

$$\alpha_3 = -\frac{1}{3} \cdot \alpha_2 = \frac{1}{6 \cdot U_T^2} \cdot \frac{g_m}{1+g_m P_E} \cdot (1 - g_m \cdot U_E)$$

TK-05.

$$U_{BE} = U_{BE} + I_c \cdot P_E -$$

$$= U_{BE} + U_T \ln \left( \frac{I_a}{I_c} \right) + I_c \cdot P_E$$

$$U_{BE} = U_{BE} + I_c \exp \left( \frac{U_{BE}}{U_T} \right) \cdot P_E$$

$$\rightarrow 0 = I_c \exp \left( \frac{U_{BE} - P_E \cdot I_a}{U_T} \right) - I_a$$

$$\text{man. } 1 - 2g_m \cdot P_E = 0.$$

$$g_m = \frac{1}{2P_E} = \frac{I_0}{U_T} \Rightarrow I_0 = \frac{U_T}{2P_E}$$

由此法也可以先将  $U_{BE} = b_1 + b_2 \ln a^2 + b_3 \ln a^3$

再将  $a_1, a_2, a_3, g_m$  对  $g_m$  求导数更快。